

**SECOND SEMESTER DIPLOMA EXAMINATION IN ELECTRICAL  
AND ELECTRONICS ENGINEERING — MARCH, 2016**

**BASIC ELECTRICAL ENGINEERING**

[Time : 3 hours

(Maximum marks : 100)

PART — A

(Maximum marks : 10)

Marks

I Answer the following questions in one or two sentences. Each question carries 2 marks.

1. Define temperature co-efficient of resistance.
2. Four  $1\Omega$  resistances are connected in parallel. What is the equivalent resistance ?
3. If charge  $Q = 144 \mu\text{C}$  and capacitance  $C = 6 \mu\text{F}$ , find voltage  $V$ .
4. Define reluctance and state its unit.
5. Write the units of magnetic flux and mmf. (5×2 = 10)

PART— B

(Maximum marks : 30)

II Answer *any five* questions from the following. Each question carries 6 marks.

1. A heater wire of length 50cm and  $1\text{mm}^2$  in cross-section carries a current of 2A when connected across a 2V battery. What is the resistivity of the wire ?
2. Draw a DC network and write mesh equations applying Kirchhoff's voltage law.
3. A current of 20A goes through two ammeters A and B connected in series. The p.d across A is 0.2V and across B is 0.3V. Find how the same current will divide between A and B when they are connected in parallel ?
4. State and explain reciprocity theorem.
5. State and explain the laws of electrostatics.
6. State Faradays laws of electromagnetic induction.
7. Draw B-H curve and mark the various regions in the graph.

(5×6 = 30)

## PART — C

(Maximum marks : 60)

(Answer *one* full question from each unit. Each full question carries 15 marks.)

## UNIT — I


- III (a) State Ohm's law. 3
- (b) Draw atomic structure of copper atom. Atomic number = 29, atomic weight = 64. 3
- (c) A wheatstone bridge circuit has  $R_{AB} = 60\Omega = R_{CD}$ ,  $R_{BC} = R_{AD} = 40\Omega$ ,  $R_{BD} = 100\Omega$ . Supply is connected to points A and C. If the current drawn from the supply is 100mA, find the currents through  $R_{BC}$ ,  $R_{CD}$  and  $R_{BD}$ . 9

OR

- IV (a) Define electric power. Write the relationship between V, I, R and P. 3
- (b) Calculate the energy spent for a 60W lamp working 8 hours day for one year. 3
- (c) Two conductors, one of copper and the other of iron, are connected in parallel and at  $20^\circ\text{C}$  carry equal currents. What proportion of current will pass through each, if the temperature is raised to  $100^\circ\text{C}$ . Assume  $\alpha$  for copper as 0.0042 and for iron as 0.006 per  $^\circ\text{C}$  at  $20^\circ\text{C}$ . 9
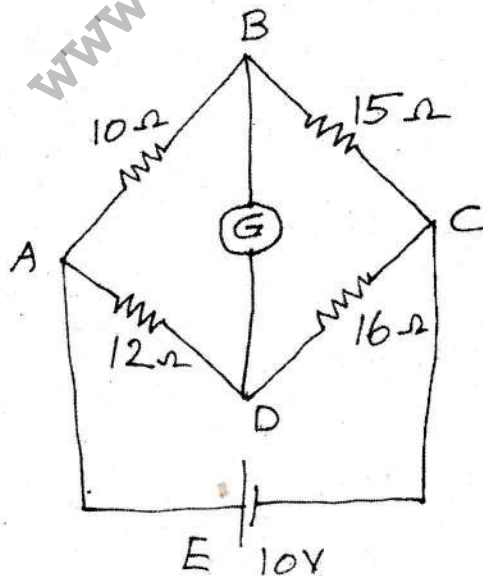
## UNIT — II


- V (a) Write any three properties of series circuit. 3
- (b) State super position theorem. 3
- (c) The galvanometer in figure below has a resistance of  $5\Omega$ . Find the current through the Galvanometer using Thevenin's Theorem.



9

OR

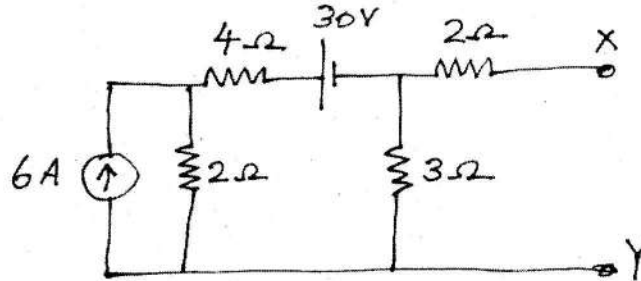- VI (a) Write any three properties of parallel circuit. 3  
 (b) State max. power transfer theorem. 3  
 (c) Find Norton's equivalent for the network to the left of terminals X-Y in figure shown below.



9

## UNIT - III

- VII (a) What is meant by dielectric strength of a medium ? 3  
 (b) Relative permittivity of mica is 5. What is its absolute permittivity ? 3  
 (c) A 10  $\mu\text{F}$ , 20  $\mu\text{F}$  and a 40  $\mu\text{F}$  capacitors are connected in series to a 399 volt source emf.  
 (i) What is the equivalent capacitance ?  
 (ii) What is the magnitude of charge across each capacitor ?  
 (iii) What is the potential difference across each capacitor ? 9

OR

- VIII (a) Write any three applications of capacitors. 3  
 (b) Calculate the total capacitance, if three capacitors of capacitance 2  $\mu\text{F}$ , 4  $\mu\text{F}$  and 6  $\mu\text{F}$  are connected in  
 (i) Series (ii) Parallel 3  
 (c) Derive the expression for energy stored in a capacitor. 9

## UNIT - IV

- IX (a) State Fleming's left hand rule. 3  
 (b) State Lenz's law. 3  
 (c) A mild steel ring having a cross-sectional area of  $500\text{mm}^2$  and a mean circumference of 400mm has a coil of 200 turns wound uniformly around it.  
 Calculate :  
 (i) The reluctance of the ring  
 (ii) The current required to produce a flux of 800  $\mu\text{Wb}$  in the ring.  
 Take relative permeability of mild steel as 400 at the given flux density. 9

OR

- X (a) Define self inductance. 3  
 (b) State Fleming's right hand rule. 3  
 (c) Derive expression for self inductance and mutual inductance. 9